


# Lecture 3: CMOS Logic

CSCSE 5730

Digital CMOS VLSI Design


**Instructor:** Saraju P. Mohanty, Ph. D.

 **NOTE:** The figures, text etc included in slides are borrowed from various books, websites, authors pages, and other sources for academic purpose only. The instructor does not claim any originality.




# Lecture Outline

- MOS Transistors
- CMOS Logic

 

 
# Introduction

- Integrated circuits: many transistors on one chip.
- *Very Large Scale Integration (VLSI)*: very many
- *Complementary Metal Oxide Semiconductor*
  - Fast, cheap, low power transistors
- How to build your own simple CMOS chip
  - CMOS transistors
  - Building logic gates from transistors
  - Transistor layout and fabrication





# Silicon

 

 
 
# Silicon Lattice

- Transistors are built on a silicon substrate.
- Silicon is a Group IV material.
- Forms crystal lattice with bonds to four neighbors.


  
# Dopants

- Silicon is a semiconductor.
- Pure silicon has no free carriers and conducts poorly.
- Adding dopants increases the conductivity.
- Group V: extra electron (n-type).
- Group III: missing electron, called hole (p-type).




# Why Silicon?


Could any other group IV metal serve purpose ?

Key Advantages:

 - Available abundantly in nature.
- Has excellent physical and electrical properties.
- Matured chemistry for fabrication.




# Devices

 

 
# p-n Junctions


- A junction between p-type and n-type semiconductor forms a diode.
- Current flows only in one direction.



anode          cathode


 


symbol

 

 
 
# MOS Transistor

- Four terminals: gate, source, drain, body (bulk, or substrate)
- Gate – oxide – body stack looks like a capacitor
  - Gate and body are conductors
  - $\text{SiO}_2$  (oxide) is a very good insulator
  - Called metal – oxide – semiconductor (MOS) capacitor
  - Even though gate is no longer made of metal



 
 
# NMOS Operation

- Body is commonly tied to ground (0 V).
- When the gate is at a low voltage:
  - P-type body is at low voltage
  - Source-body and drain-body diodes are OFF
  - No current flows, transistor is OFF



 
 
# NMOS Operation .....

- When the gate is at a high voltage:
  - Positive charge on gate of MOS capacitor
  - Negative charge attracted towards gate
  - Inverts a channel under gate to n-type
  - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



  
# PMOS Transistor

- Similar, but doping and voltages reversed
  - Body tied to high voltage ( $V_{DD}$ )
  - Gate low: transistor ON
  - Gate high: transistor OFF
  - Bubble indicates inverted behavior



 
# Power Supply Voltage

- $GND = 0\text{ V}$
- In 1980's,  $V_{DD} = 5\text{V}$
- $V_{DD}$  has decreased in modern processes
  - High  $V_{DD}$  would damage modern tiny transistors
  - Lower  $V_{DD}$  saves power
- $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, \dots$
- For 65nm or 45nm it is approximately 0.7V.




 
# CMOS Circuits with Transistor as Switch




 
 
# Transistors as Switches: Ideal

- We can view MOS transistors as electrically controlled switches.
- Voltage at gate controls path from source to drain.






# CMOS Inverter

| A | Y |
|---|---|
| 0 |   |
| 1 |   |

   




# CMOS Inverter

| A | Y |
|---|---|
| 0 |   |
| 1 | 0 |

   



# CMOS Inverter

| A | Y |
|---|---|
| 0 | 1 |
| 1 | 0 |

   



# CMOS NAND Gate

| A | B | Y |
|---|---|---|
| 0 | 0 |   |
| 0 | 1 |   |
| 1 | 0 |   |
| 1 | 1 |   |

  




# CMOS NAND Gate

| A        | B        | Y        |
|----------|----------|----------|
| <b>0</b> | <b>0</b> | <b>1</b> |
| 0        | 1        |          |
| 1        | 0        |          |
| 1        | 1        |          |

  




# CMOS NAND Gate

| A        | B        | Y        |
|----------|----------|----------|
| 0        | 0        | 1        |
| <b>0</b> | <b>1</b> | <b>1</b> |
| 1        | 0        |          |
| 1        | 1        |          |

   



# CMOS NAND Gate

| A        | B        | Y        |
|----------|----------|----------|
| 0        | 0        | 1        |
| 0        | 1        | 1        |
| <b>1</b> | <b>0</b> | <b>1</b> |
| 1        | 1        |          |

   




# CMOS NAND Gate

| A        | B        | Y        |
|----------|----------|----------|
| 0        | 0        | 1        |
| 0        | 1        | 1        |
| 1        | 0        | 1        |
| <b>1</b> | <b>1</b> | <b>0</b> |

  


# CMOS NOR Gate (Dual of NAND)

| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

  
 

 
# 3-input NAND / 4-input NOR Gate

- Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0




## 4-input NOR Gate

  

 
# Complementary CMOS : General

- Complementary CMOS logic gates:

- NMOS *pull-down network*
- PMOS *pull-up network*
- *a.k.a.* static CMOS





|               | Pull-up OFF | Pull-up ON  |
|---------------|-------------|-------------|
| Pull-down OFF | Z (float)   | 1           |
| Pull-down ON  | 0           | X (crowbar) |

 

 
 
# Connection and Behavior of Transistors

- NMOS: 1 = ON
- PMOS: 0 = ON
- *Series*: both must be ON
- *Parallel*: either can be ON



  
# Conduction Complement

- Complementary CMOS gates always produce 0 or 1.
- Example: NAND gate
  - Series NMOS:  $Y=0$  when both inputs are 1
  - Thus  $Y=1$  when either input is 0
  - Requires parallel PMOS
- Rule of *Conduction Complements*
  - Pull-up network is complement of pull-down
  - Parallel  $\rightarrow$  series, series  $\rightarrow$  parallel



 
# Signal Strength

- *Strength* of signal
  - How close it approximates ideal voltage source?
- $V_{DD}$  and GND rails are strongest 1 and 0.
- NMOS pass strong 0
  - But degraded or weak 1
- PMOS pass strong 1
  - But degraded or weak 0
- Thus, NMOS are best for pull-down network.
- And, PMOS are best for pull-up network.


 
# CMOS Transistor Synthesis of Boolean



- Formed using combination of series and parallel switch structures.
- *Compound gates* can do any inverting function.
- Synthesis Steps:
  - Express the function in inverting form.
  - Do NMOS realization of the new function without inverting. Series is AND and parallel is OR.
  - Do PMOS realization which is dual of NMOS. Dual means NMOS becomes PMOS, series becomes parallel and parallel becomes series.
  - Connect the NMOS and PMOS realizations. Connecting point is the output point.



# Compound Gates

  
- Example:

$$Y = \overline{A \square B + C \square D} \text{ (AND-AND-OR-INVERT )}$$




# Compound Gates ...

 Example:  $Y = \overline{(A + B + C)} \square D$













 Solve Example 6.2, page-240, Rabaey book.




# Pass Transistors

- Transistors can be used as switches.

          

 
# Transmission Gates


- Pass transistors produce degraded outputs.
- *Transmission gates* pass both 0 and 1 well.



$g = 0, gb = 1$

 


$g = 1, gb = 0$

 






Input

Output

$g = 1, gb = 0$

 




$g = 1, gb = 0$

     

# Tristate Buffer



- *Tristate buffer* produces Z when not enabled.

| EN | A | Y |
|----|---|---|
| 0  | 0 | Z |
| 0  | 1 | Z |
| 1  | 0 | 0 |
| 1  | 1 | 1 |

   

 
 
# Nonrestoring Tristate Buffer

- Transmission gate acts as tristate buffer.
  - Only two transistors
  - But *nonrestoring*
    - Noise on A is passed on to Y


  
# Tristate Inverter



- Tristate inverter produces restored output.
  - Violates conduction complement rule
  - Because we want a Z output



# Multiplexers



- 2:1 multiplexer chooses between two inputs.

| S | D1 | D0 | Y |
|---|----|----|---|
| 0 | X  | 0  | 0 |
| 0 | X  | 1  | 1 |
| 1 | 0  | X  | 0 |
| 1 | 1  | X  | 1 |

  

 
 
# Multiplexers Design : One Approach

- $Y = SD_1 + \bar{S}D_0$  (too many transistors)
- How many transistors are needed? 20




 
 
# Multiplexers Design : 2<sup>nd</sup> Approach

- Nonrestoring mux uses two transmission gates.
  - Only 4 transistors





# 4:1 Multiplexer

   - 4:1 mux chooses one of 4 inputs using two selects.
  - Two levels of 2:1 muxes
  - Or four tristates




 
 
# D Latch

- When  $CLK = 1$ , latch is *transparent*
  - D flows through to Q like a buffer
- When  $CLK = 0$ , the latch is *opaque*
  - Q holds its old value independent of D
- *a.k.a. transparent latch or level-sensitive latch.*







# D Latch : Design

- Multiplexer chooses D or old Q.

  
 


# D Latch : Operation

    


 
 
# D Flip-flop

- When CLK rises, D is copied to Q.
- At all other times, Q holds its value.
- a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop.*







# D Flip-flop : Design

- Built from master and slave D latches.

  
 


# D Flip-flop : Operation

    
  
# D-FF : Race Condition

- Back-to-back flops can malfunction from clock skew.
  - Second flip-flop fires late
  - Sees first flip-flop change and captures its result
  - Called *hold-time failure* or *race condition*



# D-FF: Nonoverlapping Clocks

- Nonoverlapping clocks can prevent races.
  - As long as nonoverlap exceeds clock skew
- We will use them in this class for safe design.
  - Industry manages skew more carefully instead

